



INSTITUTO SUPERIOR TÉCNICO

MEEC

2º SEMESTRE 2014/2015

ARQUITECTURAS AVANÇADAS DE COMPUTADORES

1º Projecto

Simulacao processador μ RISC com funcionamento
multi-ciclo

João Baúto N° 72856

João Severino N° 73608

Docente: Prof. Leonel Sousa

29 de Março de 2015

Conteúdo

1	Introdução	2
2	Arquitectura do μRISC	3
2.1	Unidade de descodificação - Decoder	3
2.2	Unidade de Armazenamento - Memória RAM/ROM partilhada	3
2.3	Unidade lógico-aritmética - ALU	3
2.3.1	Unidade Aritmética	4
2.3.2	Unidade Lógica	4
2.3.3	Unidade de Deslocamentos	5
2.4	Unidade de Constantes	5
2.5	Unidade de Controlo de saltos e <i>flags</i>	6
2.6	Esquema da Arquitectura	7
3	Conclusão	8
4	Anexos	9
4.1	Unidade de Descodificação	9
4.2	Unidade lógico-aritmética	11
4.2.1	Unidade Aritmética	11
4.2.2	Unidade Lógica	13
4.2.3	Unidade Deslocamento	14
4.3	Unidade de Constantes	15
4.4	Unidade de Controlo de saltos e <i>flags</i>	15
4.5	<i>Program Counter</i>	17
4.6	Unidade de Constantes	18
4.7	Unidade de Armazenamento Partilhada	18
4.8	Multiplexer de Selecção de saída	20
4.9	Registos do Nível ID	21
4.10	Registos do Nível ID RD	21
4.11	Registos do Nível EX MEM	23
4.12	Finite State Machine - FSM	24
4.13	Arquitectura μ RISC	27

1. Introdução

Com este trabalho, propusemo-nos a desenhar a arquitectura de um processador $\mu RISC$ com funcionamento multi-ciclo. Dividimos a arquitectura em unidades funcionais de modo a simplificar a implementação do processador.

O processador $\mu RISC$ consiste num processador com um número reduzido de instruções simples, nosso caso 42 instruções, distribuídas entre operações de salto, aritméticas, lógicas, deslocamento, *load/store* e uso de constantes.

Um processador do RISC, *Reduced Instruction Set Computer*, é o predecessor do mais aclamado CISC, *Complex Instruction Set Computer*, no qual uma instrução pode executar diversas operações de baixo nível como *ADD*, *LOAD* e *STORE*.

A reduzida complexidade do RISC garante-lhe uma grande vantagem relativamente ao CISC ao nível de *hardware* uma vez que um *instruction set* de menor complexidade requer menos lógica na decodificação. Outra vantagem é que o RISC mantém o valor nos registos enquanto que o CISC após o término de uma instrução faz *reset* aos registos.

O CISC uma vez que tem um instruction set mais complexo necessita de menos instruções de alto nível e como tal isto reflecte-se na memória ocupada para guardar as instruções. Parte do trabalho é transferido para o compilador uma vez que necessita de computação adicional a converter linguagem de alto nível para instruções que o processador compreenda.

2. Arquitectura do μ RISC

2.1 Unidade de descodificação - Decoder

Por decisão própria, na unidade de descodificação foi efectuado o máximo possível de descodificação de operações, selectores de *multiplexers* e unidades funcionais. Desta forma é nos possível generalizar as restantes unidades funcionais centralizando toda a descodificação numa só unidade. Uma consequência desta metodologia é o aumento da complexidade da unidade e o número de sinais de *output*.

O mesmo método foi aplicado para as instruções de *jump*. Uma descodificação parcial é feita no *decoder* permitindo diminuir a lógica aplicada à unidade funcional de saltos.

2.2 Unidade de Armazenamento - Memória RAM/ROM partilhada

De forma a facilitar o endereçamento da memória optou-se por uma unidade de armazenamento partilhado. No início da simulação esta é inicializada a partir de um ficheiro .txt graças à utilização de uma *impure function* que introduz as instruções a primeira posição de memória incrementando o endereço para a seguinte instrução. Esta unidade apresenta três entradas, Din para o armazenamento de dados através para instrução *store*, Addr_Instr que indica o endereço da próxima instrução a ser enviada para o *Decoder* e Addr_Dados que endereça a posição para onde será feito uma instrução de *load*. Como saídas tem-se Dout_Dados proveniente da instrução *load* e Instr que indica a próxima instrução.

As vantagens deste tipo de memória é a facilidade de endereçamento uma vez que não é necessário fornecer um offset para o caso em que é necessário aceder a um array *por exemplo*. Como desvantagem tem-se o facto de o programador necessitar de uma extra atenção às posições de memória onde guarda dos dados podendo substituir futuras instruções.

Com duas memórias independentes seria possível evitar este problema caso ambas as memórias fossem inicializadas com os mesmos dados (instruções e *arrays*).

2.3 Unidade lógico-aritmética - ALU

Desenhou-se a ALU com três unidades a funcionarem em paralelo, abaixo descritas com maior detalhe. O resultado produzido por estas unidades é introduzido num *multiplexer* que selecciona de acordo com sinais provenientes da unidade de descodificação qual o resultado e as *Flags* a colocar à saída da ALU.

2.3.1 Unidade Aritmética

A unidade Aritmética é responsável pelas operações apresentadas na tabela 2.1.

OP	Operação	Mnemónica	Flags actualizadas
00000	$C = A + B$	add c, a, b	S,C,Z,V
00001	$C = A + B + 1$	addinc c, a, b	S,C,Z,V
00011	$C = A + 1$	inca c, a	S,C,Z,V
00100	$C = A - B - 1$	subdec c, a, b	S,C,Z,V
00101	$C = A - B$	sub c, a, b	S,C,Z,V
00110	$C = A - 1$	deca c, a	S,C,Z,V

Tabela 2.1: Operações Aritméticas

A unidade aritmética começa por analisar qual a operação a executar de acordo com os dados vindos da unidade de decodificação e em seguida começa por calcular o segundo membro da operação $C = A + \text{oper}B$ em que

$$\text{oper}B = \begin{cases} B & : OP = 00000 \\ B + 1 & : OP = 00001 \\ 1 & : OP = 00011 \\ -B - 1 & : OP = 00100 \\ -B & : OP = 00101 \\ -1 & : OP = 00110 \end{cases}$$

De seguida calcula $C = A + \text{oper}B$ e as *Flags* correspondentes com base na análise do resultado e dos operandos.

2.3.2 Unidade Lógica

A unidade Lógica é responsável pelas operações apresentadas na tabela 2.2.

OP	Operação	Mnemónica	Flags actualizadas
10000	$C = 0$	zeros c	Nenhuma
10001	$C = A \& B$	and c, a, b	S,Z
10010	$C = !A \& B$	andnota c, a, b	S,Z
10011	$C = B$	passb c, b	Nenhuma
10100	$C = A \& !B$	andnotb c, a, b	S,Z
10101	$C = A$	passa c, a	S,Z
10110	$C = A \oplus B$	xor c, a, b	S,Z
10111	$C = A B$	or c, a, b	S,Z
11000	$C = !A \& !B$	nor c, a, b	S,Z
11001	$C = !(A \oplus B)$	xnor c, a, b	S,Z
11010	$C = !A$	passnota c, a	S,Z
11011	$C = !A B$	ornota c, a, b	S,Z
11100	$C = !B$	passnotb c, b	S,Z
11101	$C = !A !B$	nand c, a, b	S,Z
11111	$C = 1$	ones c	Nenhuma

Tabela 2.2: Operações de Deslocamento

2.3.3 Unidade de Deslocamentos

A unidade de Deslocamentos é responsável pelas operações apresentadas na tabela 2.3.

OP	Operação	Mnemónica	Flags actualizadas
01000	$C = ShiftLgicoEsq.(A)$	lsl c, a	S,C,Z
01001	$C = ShiftAritmticoDir.(A)$	asr c, a	S,C,Z

Tabela 2.3: Operações de Deslocamento

No caso do *shift* lógico a saída resulta do deslocamento do sinal de entrada uma posição e preenchimento do *bit0* com 0. No caso do *shift* aritmético a saída resulta do deslocamento do sinal de entrada uma posição e preenchimento do *bit15* com o *bit15* da entrada.

2.4 Unidade de Constantes

A unidade de Constantes é responsável pelas operações apresentadas na tabela 2.4.

Optámos por separar estas operações das restantes da ALU de modo a facilitar a decodificação das instruções por parte do *Decoder* e uma vez que o caminho crítico é devido à elevada complexidade da ALU a separação desta unidade funcional da ALU não tem qualquer tipo de influência na frequência de relógio.

Formato	Operação	Mnemónica
I	$C = Constante$	loadlit c, Const
II	$C = Const8 (C\&0xff00)$	lcl c, Const8
II	$C = (Const8 < 8) (C\&0x00ff)$	lch c, Const8

Tabela 2.4: Operações com Constantes

2.5 Unidade de Controlo de saltos e *flags*

Desenhou-se a unidade de modo a controlar o próximo endereço a enviar ao *Program Counter* (PC). Esta unidade guarda os valores das *flags* provenientes da ALU em registos e depois usa esses registos para calcular as condições de salto.

Juntámos os registos das *flags* com a unidade de controlo de saltos de modo a que consoante a condição de salto vinda do *Decoder* se pudesse calcular se se deveria executar um salto ou se permitíamos que o valor do *PC* fosse incrementado normalmente.

O cálculo do próximo endereço do *PC* é feito em 4 fases.

1. Cálculo da condição de salto
2. Cálculo do *offset* para o caso de saltos no Formato I ou do Formato II
3. Determinar se o salto é para um *offset* ou para um registo
4. Determinar o próximo endereço do *PC* com base no tipo de *jump* (condicional ou incondicional) e a condição

$$\text{Condição} = \left\{ \begin{array}{ll} 1 & : \text{COND} = 0000 \\ \text{flagV} & : \text{COND} = 0011 \\ \text{flagS} & : \text{COND} = 0100 \\ \text{flagZ} & : \text{COND} = 0101 \\ \text{flagC} & : \text{COND} = 0110 \\ \text{flagS} + \text{flagZ} & : \text{COND} = 0111 \\ 0 & : \text{others} \end{array} \right.$$

$$\text{Offset} = \left\{ \begin{array}{ll} \text{Destino}(11)\&\text{Destino}(11)\&\text{Destino}(11)\&\text{Destino}(11) & : \text{OP} = 10 \\ &\&\text{Destino}(11 \text{ downto } 0) \\ \text{Destino}(7)\&\text{Destino}(7)\&\text{Destino}(7)\&\text{Destino}(7)\&\text{Destino}(7) & : \text{others} \\ &\&\text{Destino}(7)\&\text{Destino}(7)\&\text{Destino}(7)\&\text{Destino}(7 \text{ downto } 0) \end{array} \right.$$

$$\text{Jump Address} = \begin{cases} RB & : OP = 11 \\ PC + 1 + Offset & : others \end{cases}$$

$$\text{Próximo PC} = \begin{cases} \text{Jump Address} & : enable_jump = 1 \cdot (\text{Condição} \oplus OP(0)) = 1 \\ \text{Jump Address} & : enable_jump = 1 \cdot OP(1) = 1 \\ PC + 1 & : others \end{cases}$$

2.6 Esquema da Arquitectura

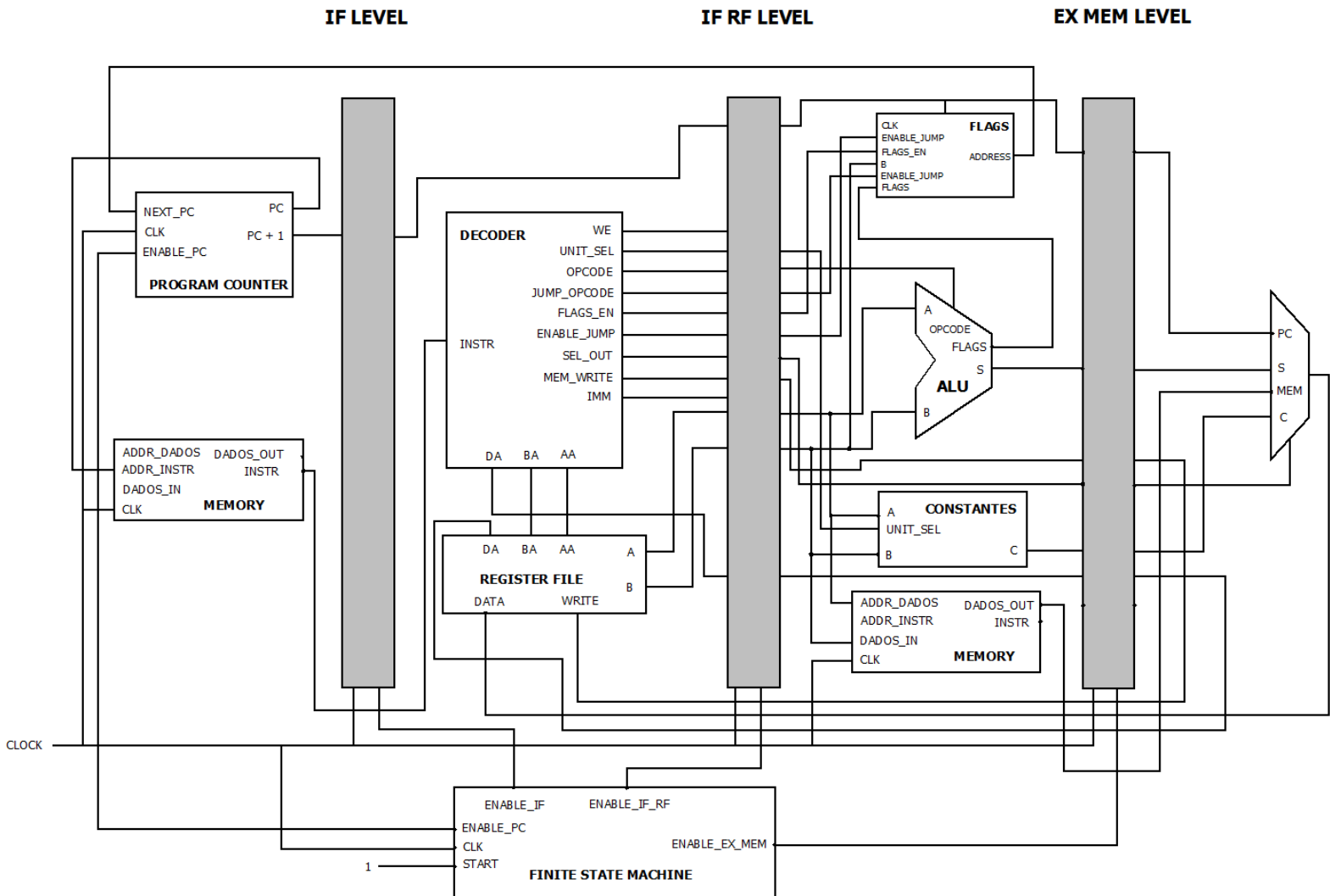


Figura 2.1: Arquitectura μ RISC.

3. Conclusão

No decorrer do trabalho deparámo-nos com algumas dificuldades, nomeadamente o carregamento dos dados de um ficheiro de entrada para a memória do processador.

Para ultrapassarmos esta dificuldade recorreremos à utilização de uma *impure function* tal como descrito na secção da Unidade de Armazenamento.

Outra unidade que nos apresentou dificuldades na sua execução foi a Unidade de Descodificação que pela sua complexidade demorou mais tempo a ser executada.

Apesar das dificuldades que nos apresentou, a Unidade de Descodificação poderia ser melhorada, fazendo com que a descodificação feita na Unidade de Saltos se juntasse ao resto da descodificação.

No geral, consideramos que o trabalho prosseguiu de acordo com o planeado.

4. Anexos

4.1 Unidade de Descodificação

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity decoder is
    Port ( INSTRUCTION : in STD_LOGIC_VECTOR (15 downto 0);
          IMM : out STD_LOGIC_VECTOR (15 downto 0); -- 10-0 quando 01XXX; 7-0 quando 11XXX
          OPCODE : out STD_LOGIC_VECTOR (4 downto 0);
          UNIT_SEL : out STD_LOGIC_VECTOR(1 downto 0);
          DA : out STD_LOGIC_VECTOR(2 downto 0);
          AA : out STD_LOGIC_VECTOR(2 downto 0);
          BA : out STD_LOGIC_VECTOR(2 downto 0);
          WE : out STD_LOGIC;
          SEL_OUT : out STD_LOGIC_VECTOR(1 downto 0);
          MEM_WRITE : out STD_LOGIC;
          jump_opcode : out STD_LOGIC_VECTOR(13 downto 0);
          flags_en : out STD_LOGIC_VECTOR(3 downto 0);
          enable_jump : out STD_LOGIC
        );
end decoder;

architecture Behavioral of decoder is
    signal instruct : STD_LOGIC_VECTOR(15 downto 0);
    signal format : STD_LOGIC_VECTOR(1 downto 0);
    signal imm_temp : STD_LOGIC_VECTOR(15 downto 0);
begin
    instruct <= INSTRUCTION;
    format <= instruct(15) & instruct(14);
    jump_opcode <= instruct(13 downto 0);

    --select unit inside alu
```

```

UNIT_SEL <= instruct(10 downto 9) when format = "10" else
    instruct(15) & instruct(10) when format = "11" or format = "01" else
    (others =>'0');

DA <= (others => '1') when instruct(15 downto 11)="00110" else
    instruct(13 downto 11);

AA <= instruct(13 downto 11) when format = "01" or format = "11" else
    instruct(5 downto 3);

BA <= instruct(2 downto 0);

OPCODE <= instruct(10 downto 6) when format = "10" or format = "00" else
    (others =>'0');

imm_temp(10 downto 0) <= instruct(10 downto 0) when format = "01" else
    instruct(7) & instruct(7) & instruct(7) & instruct(7 downto 0) when format =
        "11" else
    (others =>'0');

imm_temp(15 downto 11) <= (others => imm_temp(10));
IMM <= imm_temp;

--write enable for register file
WE <= '1' when instruct(15 downto 11)="00110" else -- Jump and Link
    '1' when instruct(15 downto 14)="10" and instruct(10 downto 6)="01010" else -- load c, a
    '1' when instruct(15 downto 14)="01" or instruct(15 downto 14)="11" else -- Constantes
    '1' when instruct(15 downto 14)="10" and instruct(10 downto 7)/="0101" else -- ALU
    '0';

--write back mux select
SEL_OUT <= "00" when instruct(15 downto 14)="10" and instruct(10 downto 7) /= "0101" else --ALU
    "01" when instruct(15 downto 14)="10" else --MEM
    "10" when instruct(14)='1' else --Const
    "11"; --PC

--flags_enable
--Z
flags_en(3) <='0' when instruct(15 downto 14)/="10" else
    '0' when instruct(10 downto 7)="0101" else
    '0' when instruct(10 downto 6)="10000" else
    '0' when instruct(10 downto 6)="10011" else

```

```

        '0' when instruct(10 downto 6)="1111" else
        '1';

--S
flags_en(2) <='0' when instruct(15 downto 14)/="10" else
        '0' when instruct(10 downto 7)="0101" else
        '0' when instruct(10 downto 6)="1000" else
        '0' when instruct(10 downto 6)="1001" else
        '0' when instruct(10 downto 6)="1111" else
        '1';

--C
flags_en(1) <='0' when instruct(15 downto 14)/="10" else
        '0' when instruct(10 downto 7)="0101" else
        '0' when instruct(10)= '1' else
        '1';

--V
flags_en(0) <='1' when instruct(15 downto 14)="10" and instruct(10 downto 9)="00" else
        '0';

enable_jump <= '1' when instruct(15 downto 14)="00" else
        '0';

MEM_WRITE <= '1' when format = "10" and instruct(10 downto 6) = "0101" else
        '0';

end Behavioral;

```

4.2 Unidade lógico-aritmética

4.2.1 Unidade Aritmética

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity arithmetic_unit is
    Port ( A : in STD_LOGIC_VECTOR (15 downto 0);

```

```

        B : in STD_LOGIC_VECTOR (15 downto 0);
        C : out STD_LOGIC_VECTOR (15 downto 0);
        OP : in STD_LOGIC_VECTOR (2 downto 0);
        Flags : out STD_LOGIC_VECTOR (3 downto 0)); --ZSCV
end arithmetic_unit;

architecture Behavioral of arithmetic_unit is
    signal C_extra : STD_LOGIC_VECTOR (16 downto 0);
    signal operB, operB2, Cin : STD_LOGIC_VECTOR (15 downto 0);
begin
    -- C_extra <= A+B when OP="000" else
    --   A+B+1 when OP="001" else
    --   A+1 when OP="011" else
    --   A-B-1 when OP="100" else
    --   A-B when OP="101" else
    --   A-1;

    operB <= B when OP(2 downto 1)="00" else
        -B when OP(2 downto 1)="10" else
        (others=>'0');
    Cin <= X"0001" when OP(2)='0' and OP(0)='1' else
        X"FFFF" when OP(2)='1' and OP(0)='0' else
        (others=>'0');
    operB2 <= operB+Cin;
    C_extra <= ('0' & A)+('0' & operB2);

    C <= C_extra(15 downto 0);

    --Zero
    Flags(3) <= not(C_extra(15) or C_extra(14) or C_extra(13) or C_extra(12) or C_extra(11) or C_extra(10)
        or C_extra(9) or C_extra(8) or C_extra(7) or C_extra(6) or C_extra(5) or C_extra(4) or C_extra(3)
        or C_extra(2) or C_extra(1) or C_extra(0));

    --Sign
    Flags(2) <= C_extra(15);

    --Carry
    Flags(1) <= C_extra(16);

    --oVerflow
    Flags(0) <= ((A(15) xnor operB2(15)) and (A(15) xor C_extra(15))) or ((operB(15) xnor Cin(15)) and
        (operB(15) xor operB2(15)));

end Behavioral;

```

4.2.2 Unidade Lógica

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity logic_unit is
    Port (A : in STD_LOGIC_VECTOR (15 downto 0);
          B : in STD_LOGIC_VECTOR (15 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0);
          OP : in STD_LOGIC_VECTOR (3 downto 0);
          Flags : out STD_LOGIC_VECTOR (3 downto 0)); --ZSCV
end logic_unit;

architecture Behavioral of logic_unit is
    signal C_intern : STD_LOGIC_VECTOR (15 downto 0);
begin
    C_intern <= (others => '0') when OP="0000" else
        A and B when OP="0001" else
        not(A) and B when OP="0010" else
        B when OP="0011" else
        A and not(B) when OP="0100" else
        A when OP="0101" else
        A xor B when OP="0110" else
        A or B when OP="0111" else
        not(A) and not(B) when OP="1000" else
        not(A xor B) when OP="1001" else
        not(A) when OP="1010" else
        not(A) or B when OP="1011" else
        not(B) when OP="1100" else
        A or not(B) when OP="1101" else
        not(A) or not(B) when OP="1110" else
        (others => '1');

    C <= C_intern;

    --Zero
    Flags(3) <= not(C_intern(15) or C_intern(14) or C_intern(13) or C_intern(12) or C_intern(11) or
```

```

        C_intern(10) or C_intern(9) or C_intern(8) or C_intern(7) or C_intern(6) or C_intern(5) or
        C_intern(4) or C_intern(3) or C_intern(2) or C_intern(1) or C_intern(0));
--Sign
Flags(2) <= C_intern(15);
--Carry
Flags(1) <= '0';
--oVerflow
Flags(0) <= '0';

end Behavioral;

```

4.2.3 Unidade Deslocamento

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity arith_logic_shift is
    Port (A : in STD_LOGIC_VECTOR (15 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0);
          OP : in STD_LOGIC;
          Flags : out STD_LOGIC_VECTOR (3 downto 0)); --ZSCV
end arith_logic_shift;

architecture Behavioral of arith_logic_shift is
    signal C_intern : STD_LOGIC_VECTOR (15 downto 0);
begin
    C_intern <= A(14 downto 0) & '0' when OP='0' else
        A(15) & A(15 downto 1);

    C <= C_intern;

--Zero
Flags(3) <= not(C_intern(15) or C_intern(14) or C_intern(13) or C_intern(12) or C_intern(11) or
    C_intern(10) or C_intern(9) or C_intern(8) or C_intern(7) or C_intern(6) or C_intern(5) or
    C_intern(4) or C_intern(3) or C_intern(2) or C_intern(1) or C_intern(0));
--Sign
Flags(2) <= C_intern(15);
--Carry

```

```

Flags(1) <= A(15) and not(OP);
--oVerflow
Flags(0) <= '0';

end Behavioral;

```

4.3 Unidade de Constantes

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity constantes is
    Port ( Const : in STD_LOGIC_VECTOR (15 downto 0);
          C_in : in STD_LOGIC_VECTOR (15 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0);
          OP_SEL : in STD_LOGIC_VECTOR (1 downto 0));
end constantes;

architecture Behavioral of constantes is
    signal Cand : STD_LOGIC_VECTOR (15 downto 0);
begin
    Cand <= C_in and X"FF00" when OP_SEL(0)='0' else
            C_in and X"00FF";
    C <= Const when OP_SEL(1)='0' else
            X"00" & Const(7 downto 0) or Cand when OP_SEL(0)='0' else
            Const(7 downto 0) & X"00" or Cand;

end Behavioral;

```

4.4 Unidade de Controlo de saltos e *flags*

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;

```



```

use IEEE.STD_LOGIC_SIGNED.ALL;

entity Flags is
    Port ( clk : in STD_LOGIC;
          Flags : in STD_LOGIC_VECTOR (3 downto 0);
          enable_flags : in STD_LOGIC_VECTOR (3 downto 0);
          enable_jump : in STD_LOGIC;
          jump_info : in STD_LOGIC_VECTOR (13 downto 0);
          PCm1 : in STD_LOGIC_VECTOR (15 downto 0);
          RB : in STD_LOGIC_VECTOR (15 downto 0);
          output_address : out STD_LOGIC_VECTOR (15 downto 0));
end Flags;

architecture Behavioral of Flags is
    signal Z,S,C,V : STD_LOGIC := '0';
    signal Cond_Status : STD_LOGIC := '0';
    signal OP : STD_LOGIC_VECTOR(1 downto 0):= (others=>'0');
    signal COND : STD_LOGIC_VECTOR(3 downto 0):= (others=>'0');
    signal Destino : STD_LOGIC_VECTOR(15 downto 0):= (others=>'0');
    signal address : STD_LOGIC_VECTOR(15 downto 0) := (others=>'0');
    signal offset : STD_LOGIC_VECTOR(15 downto 0):= (others=>'0');
begin

    -- Flag Registers
    Z <= Flags(3) when enable_flags(3)='1' and rising_edge(clk);
    S <= Flags(2) when enable_flags(2)='1' and rising_edge(clk);
    C <= Flags(1) when enable_flags(1)='1' and rising_edge(clk);
    V <= Flags(0) when enable_flags(0)='1' and rising_edge(clk);

    OP <= jump_info(13 downto 12);
    COND <= jump_info(11 downto 8);

    Cond_Status <= '1' when COND="0000" else
        V when COND="0011" else
        S when COND="0100" else
        Z when COND="0101" else
        C when COND="0110" else
        S or Z when COND="0111" else
        '0';

    offset <= jump_info(11) & jump_info(11) & jump_info(11) & jump_info(11) & jump_info(11 downto 0) when
        OP="10" else

```

```

        jump_info(7) & jump_info(7) & jump_info(7) & jump_info(7) & jump_info(7) & jump_info(7) &
        jump_info(7) & jump_info(7) & jump_info(7 downto 0);

Destino <= RB when OP="11" else
    PCm1 + offset;

address <= Destino when enable_jump='1' and (Cond_Status xnor OP(0))='1' else
    Destino when enable_jump='1' and OP(1)='1' else
    PCm1;

output_address <= address;

end Behavioral;

```

4.5 *Program Counter*

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity ProgramCounter is
    Port ( next_PC : in STD_LOGIC_VECTOR (15 downto 0);
          enable_pc : in STD_LOGIC;
          PC : out STD_LOGIC_VECTOR (15 downto 0);
          PCm1 : out STD_LOGIC_VECTOR (15 downto 0);
          clk : in STD_LOGIC);
end ProgramCounter;

architecture Behavioral of ProgramCounter is
    signal currentPC : STD_LOGIC_VECTOR (15 downto 0) := (others =>'0');
begin
    process(clk,enable_pc)
    begin
        if enable_pc='1' and rising_edge(clk) then
            currentPC <= next_PC;
        end if;
    end process;

    PC <= currentPC;

```

```

PCm1 <= currentPC+1;

end Behavioral;

```

4.6 Unidade de Constantes

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity constantes is
    Port ( Const : in STD_LOGIC_VECTOR (15 downto 0);
          C_in : in STD_LOGIC_VECTOR (15 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0);
          OP_SEL : in STD_LOGIC_VECTOR (1 downto 0));
end constantes;

architecture Behavioral of constantes is
    signal Cand : STD_LOGIC_VECTOR (15 downto 0);
begin
    Cand <= C_in and X"FF00" when OP_SEL(0)='0' else
            C_in and X"00FF";
    C <= Const when OP_SEL(1)='0' else
            X"00" & Const(7 downto 0) or Cand when OP_SEL(0)='0' else
            Const(7 downto 0) & X"00" or Cand;

end Behavioral;

```

4.7 Unidade de Armazenamento Partilhada

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use STD.TEXTIO.all;
use STD.TEXTIO;

```

```

use IEEE.STD_LOGIC_TEXTIO.all;

entity rom_instrc is
  port(clk : in std_logic;

        we : in std_logic;
        addr_instr : in std_logic_vector(15 downto 0);
        addr_dados : in std_logic_vector(15 downto 0);
        din : in std_logic_vector(15 downto 0);
        dout_instr : out std_logic_vector(15 downto 0);
        dout_dados : out std_logic_vector(15 downto 0);
        print : out std_logic);
end rom_instrc;

architecture Behavioral of rom_instrc is
  type RamType is array(0 to 65535) of STD_LOGIC_VECTOR(15 downto 0);
  impure function InitRamFromFile (RamFileName : in string) return RamType is
    file INFILE : TEXT is in "demo_lab1_3.txt";
    variable DATA_TEMP : STD_LOGIC_VECTOR(15 downto 0);
    variable IN_LINE: LINE;
    variable RAM : RamType;
    variable index :integer;

    begin
      index := 0;
      while NOT(endfile(INFILE)) loop
        readline(INFILE,IN_LINE);
        hread(IN_LINE, DATA_TEMP);
        RAM(index) := DATA_TEMP;
        index := index + 1;
      end loop;
      for index in index to 65535 loop
        RAM(index) := X"0000";
      end loop;
    return RAM;
  end function;

  signal RAM : RamType := InitRamFromFile("demo_lab1_3.txt");
  --signal teste : integer := InitRamToFile(RAM);
  signal dados : STD_LOGIC_VECTOR(15 downto 0);

```

```

signal instr: STD_LOGIC_VECTOR(15 downto 0);
begin
  process (clk)
  begin
    if clk'event and clk = '1' then
      if we = '1' then
        RAM(conv_integer(dados)) <= din;
      end if;
      dout_instr <= RAM(conv_integer(instr)); -- REVER
      dout_dados <= RAM(conv_integer(dados)); -- REVER
    end if;
  end process;

  dados <= addr_dados(15 downto 0);
  instr <= addr_instr(15 downto 0);
  print <= '1' when RAM(conv_integer(instr)) = X"2FFF" else
    '0';

end Behavioral;

```

4.8 Multiplexer de Selecção de saída

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.NUMERIC_STD.ALL;
use IEEE.STD_LOGIC_SIGNED.ALL;

entity writeback_mux is
  Port (ALU : in STD_LOGIC_VECTOR (15 downto 0);
        MEM : in STD_LOGIC_VECTOR (15 downto 0);
        Consts : in STD_LOGIC_VECTOR (15 downto 0);
        PC : in STD_LOGIC_VECTOR (15 downto 0);
        Sel_WB : in STD_LOGIC_VECTOR (1 downto 0);
        C : out STD_LOGIC_VECTOR (15 downto 0)
        );
end writeback_mux;

architecture Behavioral of writeback_mux is

```

```

begin

    C <= ALU when Sel_WB="00" else
        MEM when Sel_WB="01" else
        Consts when Sel_WB="10" else
        PC;

end Behavioral;

```

4.9 Registos do Nível ID

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity IF_Regs is
    Port (Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
          Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
          clk : in STD_LOGIC;
          enable : in STD_LOGIC
          );
end IF_Regs;

architecture Behavioral of IF_Regs is
begin
    process (clk)
    begin
        if clk'event and clk='1' then
            if enable = '1' then
                Next_PC_out <= Next_PC_in;
            end if;
        end if;
    end process;

end Behavioral;

```

4.10 Registos do Nível ID RD

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ID_RF_Regs is
    Port (Current_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
          Current_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
          Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
          Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
          IMM_in : in STD_LOGIC_VECTOR (15 downto 0);
          IMM_out : out STD_LOGIC_VECTOR (15 downto 0);
          OPCODE_in : in STD_LOGIC_VECTOR (4 downto 0);
          OPCODE_out : out STD_LOGIC_VECTOR (4 downto 0);
          UNIT_SEL_in : in STD_LOGIC_VECTOR (1 downto 0);
          UNIT_SEL_out : out STD_LOGIC_VECTOR (1 downto 0);
          DA_in : in STD_LOGIC_VECTOR (2 downto 0);
          DA_out : out STD_LOGIC_VECTOR (2 downto 0);
          A_in : in STD_LOGIC_VECTOR (15 downto 0);
          A_out : out STD_LOGIC_VECTOR (15 downto 0);
          B_in : in STD_LOGIC_VECTOR (15 downto 0);
          B_out : out STD_LOGIC_VECTOR (15 downto 0);
          WE_in : in STD_LOGIC;
          WE_out : out STD_LOGIC;
          SEL_OUT_in : in STD_LOGIC_VECTOR (1 downto 0);
          SEL_OUT_out : out STD_LOGIC_VECTOR (1 downto 0);
          MEM_WRITE_in : in STD_LOGIC;
          MEM_WRITE_out : out STD_LOGIC;
          jump_opcode_in : in STD_LOGIC_VECTOR (13 downto 0);
          jump_opcode_out : out STD_LOGIC_VECTOR (13 downto 0);
          flags_en_in : in STD_LOGIC_VECTOR (3 downto 0);
          flags_en_out : out STD_LOGIC_VECTOR (3 downto 0);
          enable_jump_in : in STD_LOGIC;
          enable_jump_out : out STD_LOGIC;
          clk : in STD_LOGIC;
          enable : in STD_LOGIC);
end ID_RF_Regs;

architecture Behavioral of ID_RF_Regs is
begin
    process (clk)
    begin

```

```

if clk'event and clk='1' then
  if enable = '1' then
    Current_PC_out <= Current_PC_in;
    Next_PC_out <= Next_PC_in;
    OPCODE_out <= OPCODE_in;
    IMM_out <= IMM_in;
    UNIT_SEL_out <= UNIT_SEL_in;
    A_out <= A_in;
    B_out <= B_in;
    WE_out <= WE_in;
    SEL_OUT_out <= SEL_OUT_in;
    MEM_WRITE_out <= MEM_WRITE_in;
    jump_opcode_out <= jump_opcode_in;
    flags_en_out <= flags_en_in;
    enable_jump_out <= enable_jump_in;
    DA_out <= DA_in;
  end if;
end if;
end process;
end Behavioral;

```

4.11 Registos do Nível EX MEM

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EX_MEM_Regs is
  Port (Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0); --alterado
        Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0); --alterado
        C_in : in STD_LOGIC_VECTOR (15 downto 0);
        C_out : out STD_LOGIC_VECTOR (15 downto 0);
        WE_in : in STD_LOGIC;
        WE_out : out STD_LOGIC;
        S_in : in STD_LOGIC_VECTOR (15 downto 0);
        S_out : out STD_LOGIC_VECTOR (15 downto 0);
        DA_in : in STD_LOGIC_VECTOR (2 downto 0);
        DA_out : out STD_LOGIC_VECTOR (2 downto 0);
        MUX_WB_in : in STD_LOGIC_VECTOR(1 downto 0);
        MUX_WB_out : out STD_LOGIC_VECTOR(1 downto 0);

```



```

        clk : in STD_LOGIC;
        enable : in STD_LOGIC
    );
end EX_MEM_Regs;

architecture Behavioral of EX_MEM_Regs is

begin
process (clk)
begin
    if clk'event and clk='1' then
        if enable = '1' then
            Next_PC_out <= Next_PC_in; --alterado
            C_out <= C_in;
            WE_out <= WE_in;
            S_out <= S_in;
            DA_out <= DA_in;
            MUX_WB_out <= MUX_WB_in;
        end if;
    end if;
end process;

end Behavioral;

```

4.12 Finite State Machine - FSM

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use STD.TEXTIO.all;
use STD.TEXTIO;
use IEEE.STD_LOGIC_TEXTIO.all;

entity FSM_Regs is
    Port( START : in STD_LOGIC;
          PRINT : in STD_LOGIC;
          ENABLE_IF : out STD_LOGIC;
          ENABLE_IF_RF : out STD_LOGIC;
          ENABLE_EX_MEM : out STD_LOGIC;

```

```

        ENABLE_PC : out STD_LOGIC;
        CLK : in STD_LOGIC
    );
end FSM_Regs;

architecture Behavioral of FSM_Regs is
    type fsm_states is (INIT, IF_level, IF_RF_level, EX_MEM_level, WB_level, IF2_level, WR_FILE);
    signal curr_state, next_state : fsm_states;
    signal counter : integer := 0;
    signal start2 : std_logic := '1';
    signal stop_print : std_logic := '0';
begin

    process (clk)
    begin
        if clk'event and clk = '1' then
            if START = '0' then
                curr_state <= INIT;
            else
                curr_state <= next_state;
            end if;
        end if;
    end process ;

    process(curr_state, START,start2,print, stop_print)
    file output: TEXT open write_mode is "ram_out.txt";
    variable my_line : LINE;
    begin
        next_state <= curr_state;

        case curr_state is
            when INIT =>
                ENABLE_IF <= '0';
                ENABLE_PC <= '0';
                ENABLE_IF_RF <= '0';
                ENABLE_EX_MEM <= '0';

                if START = '1' and start2 = '1' then
                    next_state <= IF_level;
                end if;

                if print = '1' and stop_print = '0' then

```

```

        next_state <= WR_FILE;
    end if;

when IF_level =>
    ENABLE_IF <= '0';
    ENABLE_PC <= '0';
    ENABLE_IF_RF <= '0';
    ENABLE_EX_MEM <= '0';

    if print = '1' and stop_print = '0' then
        next_state <= WR_FILE;
    else
        next_state <= IF_RF_level;
    end if;

when IF2_level =>
    ENABLE_IF <= '0';
    ENABLE_PC <= '1';
    ENABLE_IF_RF <= '0';
    ENABLE_EX_MEM <= '0';

    if print = '1' and stop_print = '0' then
        next_state <= WR_FILE;
    else
        next_state <= IF_RF_level;
    end if;

when IF_RF_level =>
    ENABLE_IF <= '1';
    ENABLE_PC <= '0';
    ENABLE_IF_RF <= '0';
    ENABLE_EX_MEM <= '0';

    if print = '1' and stop_print = '0' then
        next_state <= WR_FILE;
    else
        next_state <= EX_MEM_level;
    end if;

when EX_MEM_level =>

    ENABLE_IF <= '0';

```

```

    ENABLE_PC <= '0';
    ENABLE_IF_RF <= '1';
    ENABLE_EX_MEM <= '0';

    if print = '1' and stop_print = '0' then
        next_state <= WR_FILE;
    else
        next_state <= WB_level;
    end if;

when WB_level =>
    ENABLE_IF <= '0';
    ENABLE_PC <= '0';
    ENABLE_IF_RF <= '0';
    ENABLE_EX_MEM <= '1';

    if print = '1' and stop_print = '0' then
        next_state <= WR_FILE;
    else
        next_state <= IF2_level;
    end if;

when WR_FILE =>
    ENABLE_IF <= '0';
    ENABLE_PC <= '0';
    ENABLE_IF_RF <= '0';
    ENABLE_EX_MEM <= '0';

    start2 <= '0';
    stop_print <= '1';
    next_state <= INIT;

end case;
end process;

end Behavioral;

```

4.13 Arquitectura μ RISC

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use work.full_memory.all;

entity cpu is
    Port( CLK, TEST1 : in STD_LOGIC;
          MEMORY : out STD_LOGIC_VECTOR(15 downto 0);
          INST_NB : out std_LOGIC_VECTOR(15 downto 0);
          PRINT : out STD_LOGIC;
          TEST: out STD_LOGIC_VECTOR(15 downto 0));
end cpu;

architecture Behavioral of cpu is
    component alu
        port(OP_SEL : in STD_LOGIC_VECTOR (4 downto 0);
              A : in STD_LOGIC_VECTOR (15 downto 0);
              B : in STD_LOGIC_VECTOR (15 downto 0);
              S : out STD_LOGIC_VECTOR (15 downto 0);
              Flags : out STD_LOGIC_VECTOR (3 downto 0));
    end component alu;

    component decoder
        port (INSTRUCTION : in STD_LOGIC_VECTOR (15 downto 0);
              IMM : out STD_LOGIC_VECTOR (15 downto 0); -- 10-0 quando 01XXX; 7-0 quando 11XXX
              OPCODE : out STD_LOGIC_VECTOR (4 downto 0);
              UNIT_SEL : out STD_LOGIC_VECTOR(1 downto 0);
              DA : out STD_LOGIC_VECTOR(2 downto 0);
              AA : out STD_LOGIC_VECTOR(2 downto 0);
              BA : out STD_LOGIC_VECTOR(2 downto 0);
              WE : out STD_LOGIC;
              SEL_OUT : out STD_LOGIC_VECTOR(1 downto 0);
              MEM_WRITE : out STD_LOGIC;
              jump_opcode : out STD_LOGIC_VECTOR(13 downto 0);
              flags_en : out STD_LOGIC_VECTOR(3 downto 0);
              enable_jump : out STD_LOGIC
        );
    end component decoder;

    component registerfile
        port(AA : in STD_LOGIC_VECTOR (2 downto 0);
              A : out STD_LOGIC_VECTOR (15 downto 0);

```

```

    BA : in STD_LOGIC_VECTOR (2 downto 0);
    B : out STD_LOGIC_VECTOR (15 downto 0);
    DA : in STD_LOGIC_VECTOR (2 downto 0);
    WE : in STD_LOGIC;
    DATA : in STD_LOGIC_VECTOR (15 downto 0);
    clk : in STD_LOGIC);
end component registerfile;

component constantes
    port(Const : in STD_LOGIC_VECTOR (15 downto 0);
          C_in : in STD_LOGIC_VECTOR (15 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0);
          OP_SEL : in STD_LOGIC_VECTOR (1 downto 0));
end component constantes;

component writeback_mux
    port(ALU : in STD_LOGIC_VECTOR (15 downto 0);
          MEM : in STD_LOGIC_VECTOR (15 downto 0);
          PC : in STD_LOGIC_VECTOR (15 downto 0);
          Consts : in STD_LOGIC_VECTOR (15 downto 0);
          Sel_WB : in STD_LOGIC_VECTOR (1 downto 0);
          C : out STD_LOGIC_VECTOR (15 downto 0));
end component writeback_mux;

component sync_ram
    port (clock : in std_logic;
          we : in std_logic;
          address : in std_logic_vector;
          datain : in std_logic_vector;
          dataout : out std_logic_vector);
end component sync_ram;

component rom_instrc
    port(clk : in std_logic;
          we : in std_logic;
          --MEM_array : out RamType;
          addr_instr : in std_logic_vector(15 downto 0);
          addr_dados : in std_logic_vector(15 downto 0);
          din : in std_logic_vector(15 downto 0);
          print : out std_logic;
          dout_instr : out std_logic_vector(15 downto 0);
          dout_dados : out std_logic_vector(15 downto 0));

```

```

end component;

component Flags
  port(clk : in STD_LOGIC;
        Flags : in STD_LOGIC_VECTOR (3 downto 0);
        enable_flags : in STD_LOGIC_VECTOR (3 downto 0);
        enable_jump : in STD_LOGIC;
        jump_info : in STD_LOGIC_VECTOR (13 downto 0);
        PCm1 : in STD_LOGIC_VECTOR (15 downto 0);
        RB : in STD_LOGIC_VECTOR (15 downto 0);
        output_address : out STD_LOGIC_VECTOR (15 downto 0));
end component Flags;

component ProgramCounter is
  port(next_PC : in STD_LOGIC_VECTOR (15 downto 0);
        enable_pc : in STD_LOGIC;
        PC : out STD_LOGIC_VECTOR (15 downto 0);
        PCm1 : out STD_LOGIC_VECTOR (15 downto 0);
        clk : in STD_LOGIC);
end component ProgramCounter;

component IF_Regs is
  Port (Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
        Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
        clk : in STD_LOGIC;
        enable : in STD_LOGIC);
end component IF_Regs;

component ID_RF_Regs is
  Port (Current_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
        Current_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
        Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
        Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
        IMM_in : in STD_LOGIC_VECTOR (15 downto 0);
        IMM_out : out STD_LOGIC_VECTOR (15 downto 0);
        OPCODE_in : in STD_LOGIC_VECTOR (4 downto 0);
        OPCODE_out : out STD_LOGIC_VECTOR (4 downto 0);
        UNIT_SEL_in : in STD_LOGIC_VECTOR (1 downto 0);
        UNIT_SEL_out : out STD_LOGIC_VECTOR (1 downto 0);
        DA_in : in STD_LOGIC_VECTOR (2 downto 0);
        DA_out : out STD_LOGIC_VECTOR (2 downto 0);
        A_in : in STD_LOGIC_VECTOR (15 downto 0);

```

```

    A_out : out STD_LOGIC_VECTOR (15 downto 0);
    B_in : in STD_LOGIC_VECTOR (15 downto 0);
    B_out : out STD_LOGIC_VECTOR (15 downto 0);
    WE_in : in STD_LOGIC;
    WE_out : out STD_LOGIC;
    SEL_OUT_in : in STD_LOGIC_VECTOR (1 downto 0);
    SEL_OUT_out : out STD_LOGIC_VECTOR (1 downto 0);
    MEM_WRITE_in : in STD_LOGIC;
    MEM_WRITE_out : out STD_LOGIC;
    jump_opcode_in : in STD_LOGIC_VECTOR (13 downto 0);
    jump_opcode_out : out STD_LOGIC_VECTOR (13 downto 0);
    flags_en_in : in STD_LOGIC_VECTOR (3 downto 0);
    flags_en_out : out STD_LOGIC_VECTOR (3 downto 0);
    enable_jump_in : in STD_LOGIC;
    enable_jump_out : out STD_LOGIC;
    clk : in STD_LOGIC;
    enable : in STD_LOGIC);
end component ID_RF_Regs;

component EX_MEM_Regs is
    Port (Next_PC_in : in STD_LOGIC_VECTOR (15 downto 0);
        Next_PC_out : out STD_LOGIC_VECTOR (15 downto 0);
        C_in : in STD_LOGIC_VECTOR (15 downto 0);
        C_out : out STD_LOGIC_VECTOR (15 downto 0);
        WE_in : in STD_LOGIC;
        WE_out : out STD_LOGIC;
        S_in : in STD_LOGIC_VECTOR (15 downto 0);
        S_out : out STD_LOGIC_VECTOR (15 downto 0);
        DA_in : in STD_LOGIC_VECTOR (2 downto 0);
        DA_out : out STD_LOGIC_VECTOR (2 downto 0);
        MUX_WB_in : in STD_LOGIC_VECTOR(1 downto 0);
        MUX_WB_out : out STD_LOGIC_VECTOR(1 downto 0);
        clk : in STD_LOGIC;
        enable : in STD_LOGIC
    );
end component EX_MEM_regs;

component FSM_Regs is
    Port( START : in STD_LOGIC;
        ENABLE_IF : out STD_LOGIC;
        ENABLE_IF_RF : out STD_LOGIC;
        ENABLE_EX_MEM : out STD_LOGIC;

```



```

    ENABLE_PC : out STD_LOGIC;
    PRINT : in STD_LOGIC;
    CLK : in STD_LOGIC
);
end component FSM_Regs;

signal opcde : STD_LOGIC_VECTOR(4 downto 0);
signal opcde_2 : STD_LOGIC_VECTOR(4 downto 0);
signal instr : STD_LOGIC_VECTOR (15 downto 0);
signal instr_2 : STD_LOGIC_VECTOR (15 downto 0);
signal imediato : STD_LOGIC_VECTOR(15 downto 0);
signal imediato_2 : STD_LOGIC_VECTOR(15 downto 0);
signal sel_unid : STD_LOGIC_VECTOR(1 downto 0);
signal sel_unid_2 : STD_LOGIC_VECTOR(1 downto 0);
signal da1,aa1,ba1 : STD_LOGIC_VECTOR(2 downto 0);
signal da1_2 : STD_LOGIC_VECTOR(2 downto 0);
signal da1_3 : STD_LOGIC_VECTOR(2 downto 0);
signal wenable : STD_LOGIC;
signal wenable_2 : STD_LOGIC;
signal wenable_3 : STD_LOGIC;
signal a_v,b_v : STD_LOGIC_VECTOR(15 downto 0);
signal a_v_2,b_v_2 : STD_LOGIC_VECTOR(15 downto 0);
signal writedata : STD_LOGIC_VECTOR(15 downto 0);
signal Flags_alu : STD_LOGIC_VECTOR(3 downto 0);
signal consts : STD_LOGIC_VECTOR(15 downto 0);
signal consts_2 : STD_LOGIC_VECTOR(15 downto 0);
signal Alu_S : STD_LOGIC_VECTOR(15 downto 0);
signal Alu_S_2 : STD_LOGIC_VECTOR(15 downto 0);
signal MUXWB : STD_LOGIC_VECTOR(1 downto 0);
signal MUXWB_2 : STD_LOGIC_VECTOR(1 downto 0);
signal MUXWB_3 : STD_LOGIC_VECTOR(1 downto 0);
signal mem_dados : STD_LOGIC_VECTOR(15 downto 0);
signal mem_dados_2 : STD_LOGIC_VECTOR(15 downto 0);
signal MEM_EN : STD_LOGIC;
signal MEM_EN_2 : STD_LOGIC;
signal jump_opc : STD_LOGIC_VECTOR(13 downto 0);
signal jump_opc_2 : STD_LOGIC_VECTOR(13 downto 0);
signal PCm1 : STD_LOGIC_VECTOR(15 downto 0);
signal PCm1_2 : STD_LOGIC_VECTOR(15 downto 0);
signal PCm1_3 : STD_LOGIC_VECTOR(15 downto 0);
signal PCm1_4 : STD_LOGIC_VECTOR(15 downto 0); --alterado
signal addr : STD_LOGIC_VECTOR(15 downto 0);

```

```

signal fl_en : STD_LOGIC_VECTOR(3 downto 0);
signal fl_en_2 : STD_LOGIC_VECTOR(3 downto 0);
signal jpen : STD_LOGIC;
signal jpen_2 : STD_LOGIC;
signal IFaddr : STD_LOGIC_VECTOR(15 downto 0);
signal IFaddr_2 : STD_LOGIC_VECTOR(15 downto 0);
signal IFaddr_3 : STD_LOGIC_VECTOR(15 downto 0);
--alterado
signal en_lv11 : STD_LOGIC;
signal en_lv12 : STD_LOGIC;
signal en_lv13 : STD_LOGIC;
signal en_pc : STD_LOGIC;
signal ram_print : STD_LOGIC;

```

```

begin

```

```

Decoder_Inst: decoder port map(
    INSTRUCTION => instr,
    OPCODE => opcode,
    IMM => immediato,
    UNIT_SEL => sel_unid,
    DA => da1,
    AA => aa1,
    BA => ba1,
    WE => wenable,
    SEL_OUT => MUXWB,
    MEM_WRITE => MEM_EN,
    jump_opcode => jump_opc,
    flags_en => fl_en,
    enable_jump => jpen
);

```

```

Constante : constantes port map(
    Const => immediato_2,
    C_in => a_v,
    C => consts,
    OP_SEL => sel_unid_2
);

```

```

RegFile : registerfile port map(
    AA => aa1,
    A => a_v,

```

```

    BA => ba1,
    B => b_v,
    DA => da1_3,
    WE => wenable_3,
    DATA => writedata,
    clk => CLK
);

ALU_OP : alu port map(
    OP_SEL => opcde_2,
    A => a_v_2,
    B => b_v_2,
    S => Alu_S,
    Flags => Flags_alu
);

WB_Mux : writeback_mux port map(
    ALU => Alu_S_2,
    MEM => mem_dados,
    Consts => consts_2,
    PC => PCm1_4,    -- alterado
    Sel_WB => MUXWB_3, -- change --> MUXWB
    C => writedata
);

RAM : rom_instrc port map(
    clk => CLK,
    we => MEM_EN_2,
    addr_instr => IFaddr,
    addr_dados => a_v_2,
    din => b_v_2,
    dout_instr => instr,
    dout_dados => mem_dados,
    print => ram_print
);

Flags_Jumps : Flags port map(
    clk => CLK,
    Flags => Flags_alu,
    enable_flags => fl_en_2,
    enable_jump => jpen_2,
    jump_info => jump_opc_2,
    PCm1 => PCm1_3,

```

```

    RB => b_v,
    output_address => addr
);

PC : ProgramCounter port map(
    next_PC => addr,
    enable_pc => en_pc,
    PC => IFaddr,
    PCm1 => PCm1,
    clk => CLK
);

IF_Registers : IF_Regs port map(
    Next_PC_in => PCm1,
    Next_PC_out => PCm1_2,
    clk => CLK,
    enable => en_lv11
);

ID_RF_Registers : ID_RF_Regs port map(
    Current_PC_in => IFaddr_2,
    Current_PC_out => IFaddr_3,
    Next_PC_in => PCm1_2,
    Next_PC_out => PCm1_3,
    IMM_in => immediato,
    IMM_out => immediato_2,
    OPCODE_in => opcode,
    OPCODE_out => opcode_2,
    UNIT_SEL_in => sel_unid,
    UNIT_SEL_out => sel_unid_2,
    DA_in => da1,
    DA_out => da1_2,
    A_in => a_v,
    A_out => a_v_2,
    B_in => b_v,
    B_out => b_v_2,
    WE_in => wenable,
    WE_out => wenable_2,
    SEL_OUT_in => MUXWB,
    SEL_OUT_out => MUXWB_2,
    MEM_WRITE_in => MEM_EN,
    MEM_WRITE_out => MEM_EN_2,

```

```

    jump_opcode_in => jump_opc,
    jump_opcode_out => jump_opc_2,
    flags_en_in => fl_en,
    flags_en_out => fl_en_2,
    enable_jump_in => jpen,
    enable_jump_out => jpen_2,
    clk => CLK,
    enable => en_lv12
);

EX_MEM_Registers : EX_MEM_Regs port map(
    WE_in => wenable_2,
    WE_out => wenable_3,
    Next_PC_in => PCm1_3, --alterado
    Next_PC_out => PCm1_4, --alterado
    C_in => consts,
    C_out => consts_2,
    S_in => Alu_S,
    S_out => Alu_S_2,
    DA_in => da1_2,
    DA_out => da1_3,
    MUX_WB_in => MUXWB_2,
    MUX_WB_out => MUXWB_3,
    clk => CLK,
    enable => en_lv13
);

FSM : FSM_Regs port map(
    START => TEST1,
    PRINT => ram_print,
    ENABLE_IF => en_lv11,
    ENABLE_IF_RF => en_lv12,
    ENABLE_EX_MEM => en_lv13,
    ENABLE_PC => en_pc,
    CLK => CLK
);

TEST <= writedata;
MEMORY <= instr;
INST_NB <= IFaddr;
PRINT <= ram_print;
end Behavioral;

```